

2

LINEAR ACTIVE FILTERS LIST

First of all some definitions and a few necessary constants:

$$k\text{rad} = 10^3 \cdot \text{rad}, M\text{rad} = 10^6 \cdot \text{rad},$$

Amplifier Gain: A_0 ,

Cut off frequency: f_0 ,

$$\text{Period: } T_0 = \frac{1}{f_0},$$

$$\text{angular frequency: } \omega_0 = 2 \cdot \pi \cdot f_0,$$

$$\text{time constant: } \tau = \frac{1}{\omega_0}$$

Quality factor: Q ,

$$\text{damping factor: } \zeta = \frac{\omega_0}{2 \cdot Q},$$


sampling frequency: f_s ,

$$\text{sampling period: } T_s = \frac{1}{f_s},$$


$$\text{sampling angular frequency: } \omega_s = 2 \cdot \pi \cdot f_s.$$

The eight basic linear active filters transfer functions (t. f.) as Laplace transforms of their impulse responses $H(t)$, (functions of the complex frequency $s=\sigma+j\omega$) are:

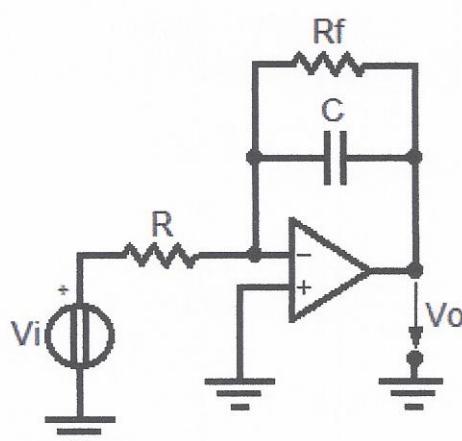
2.1) Low Pass Filter or inverting integrator (1st order): $W_1(s) = \frac{A_0 \cdot \omega_0}{s + \omega_0},$



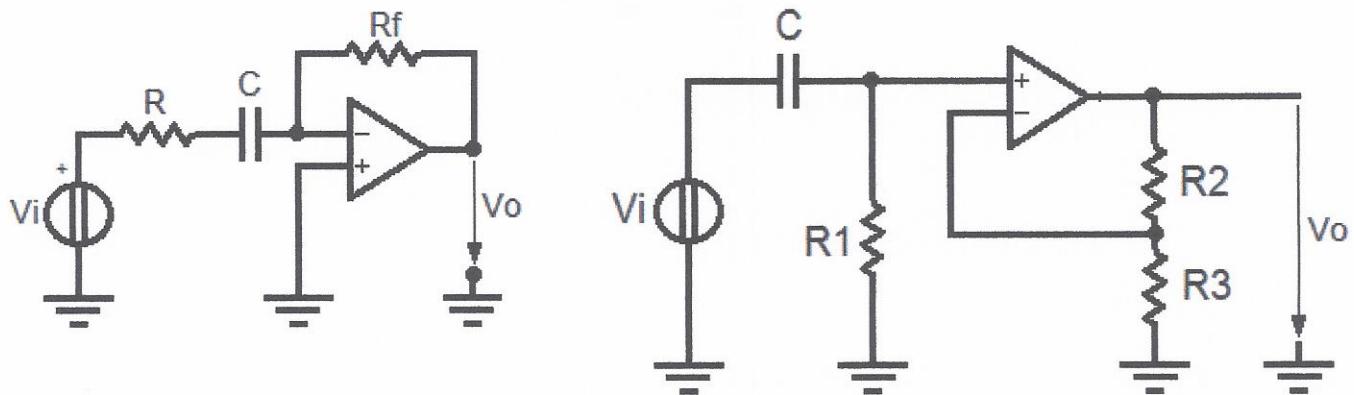
2.2) High Pass or inverting derivator (I° order): $W_2(s) = \frac{A_0 \cdot s}{s + \omega_0}$,



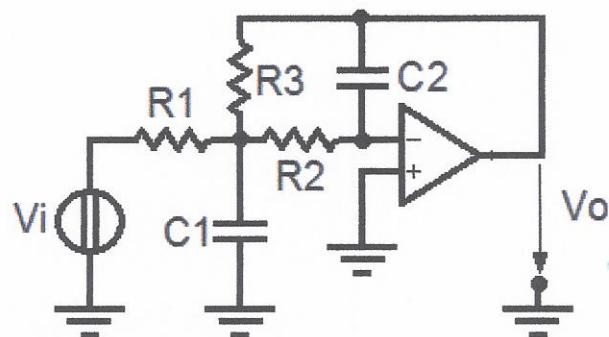
2.3) Low Pass (II° order): $W_3(s) = \frac{A_0 \cdot \omega_0^2}{s^2 + 2 \cdot \zeta \cdot s + \omega_0^2}$,



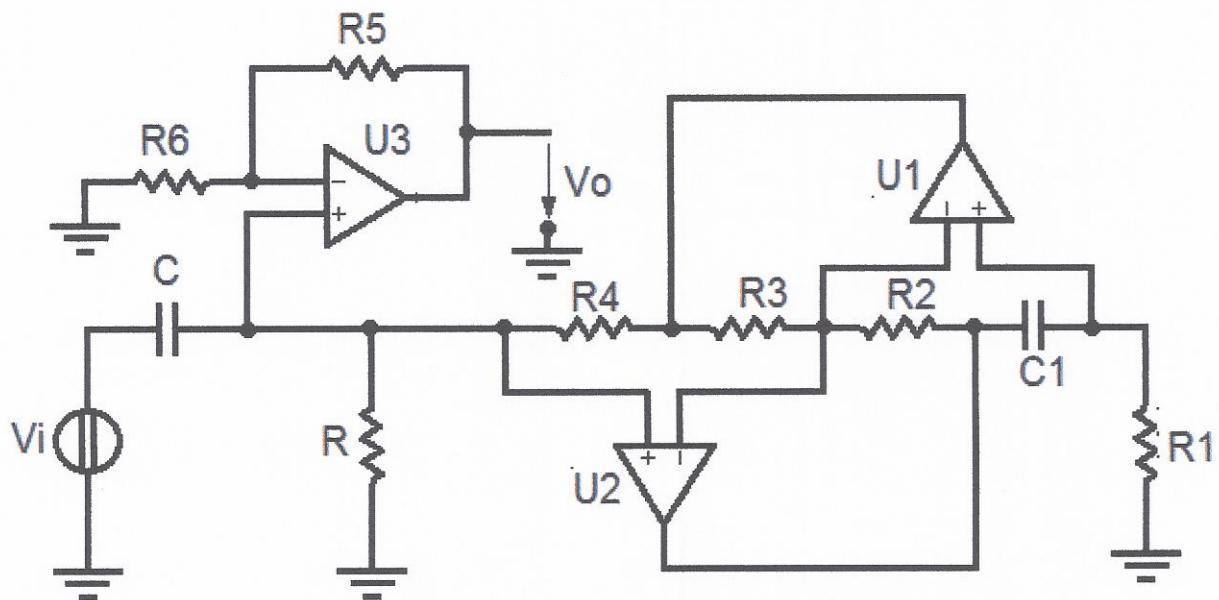
2.4) High Pass (II^oorder): $W4(s) = \frac{A_0 \cdot s^2}{s^2 + 2 \cdot \zeta \cdot s + \omega_0^2},$



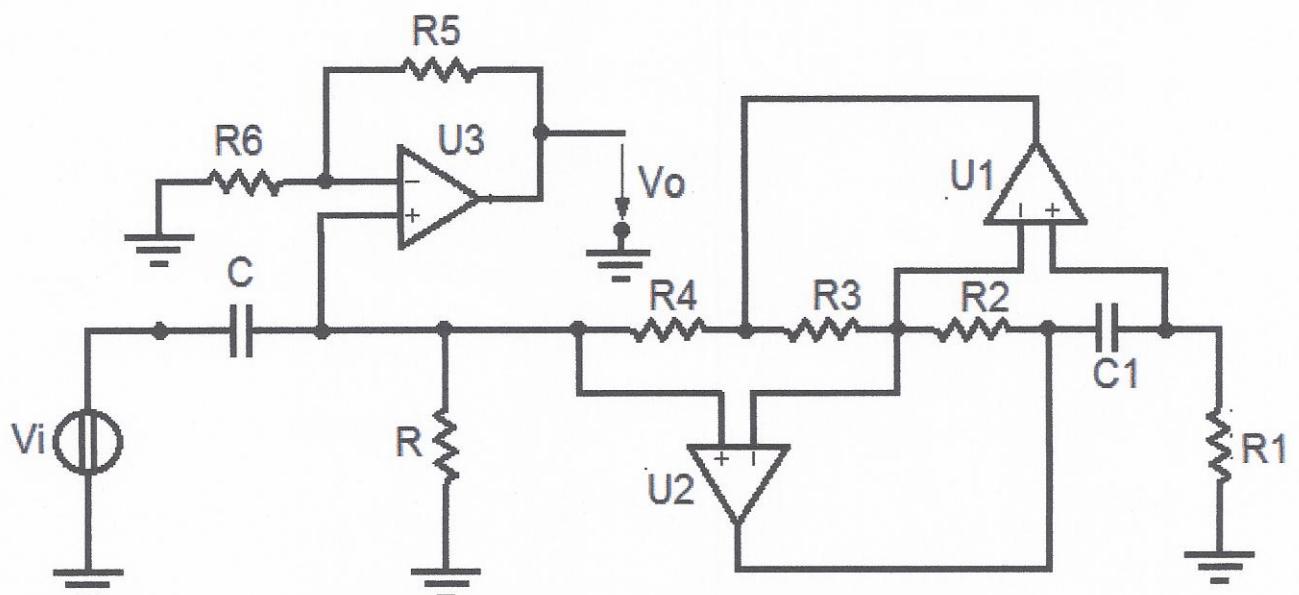2.5) Band Pass (II^oorder): $W5(s) = \frac{A_0 \cdot 2 \cdot \zeta \cdot s}{s^2 + 2 \cdot \zeta \cdot s + \omega_0^2},$




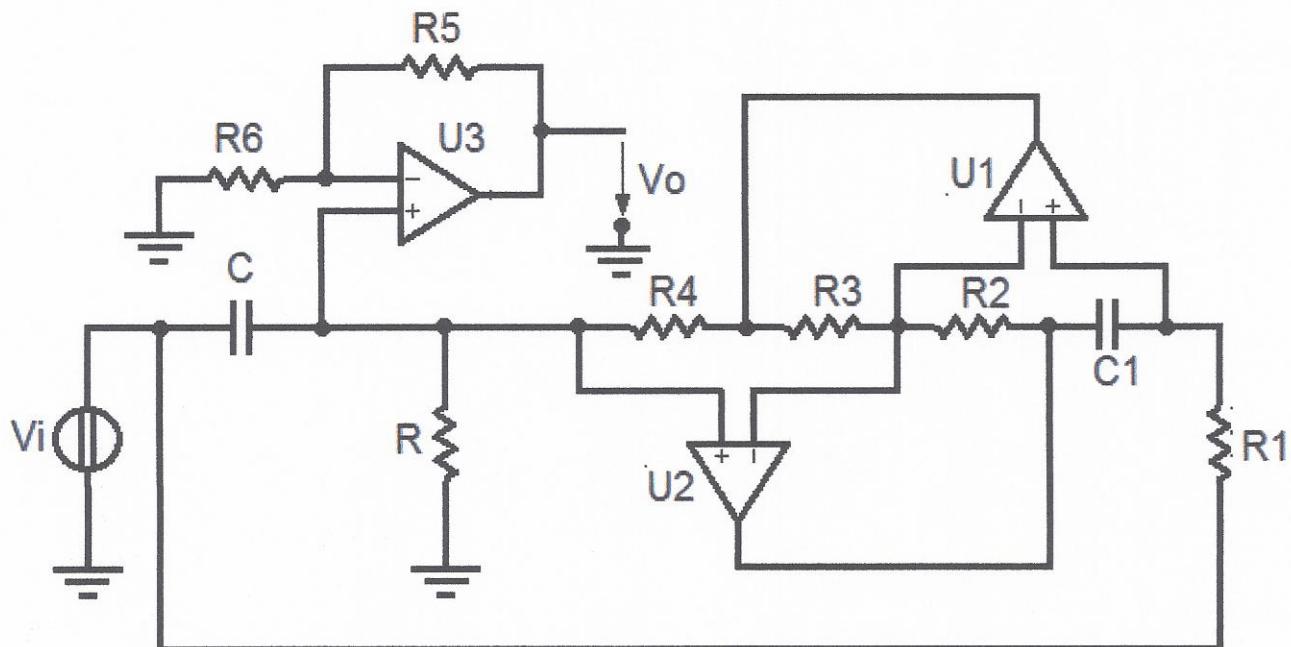2.6) Band stop (II°order): $W_6(s) = \frac{A_0 \cdot (s^2 + \omega_0^2)}{s^2 + 2 \cdot \zeta \cdot s + \omega_0^2}$,



2.7) Butterworth Filter: $W_{Bw}(s) = \frac{A_0}{Bw_n(s)}$, where we have indicated
with $Bw_n(s)$ the Butterworth polinom of nth grad.

Third Order Filter

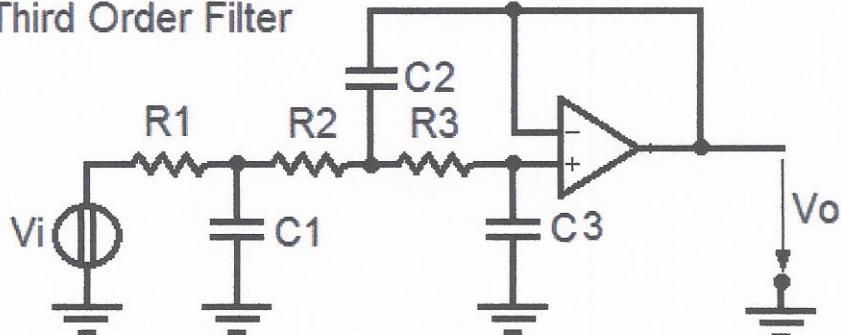

2.8) Chebyshev Filter: $W_{Ch}(s) = \frac{A_0}{T_{ch}(s)}$.
 (Starting roll-off, greater than that of Butterworth.)

Fourth order filter

