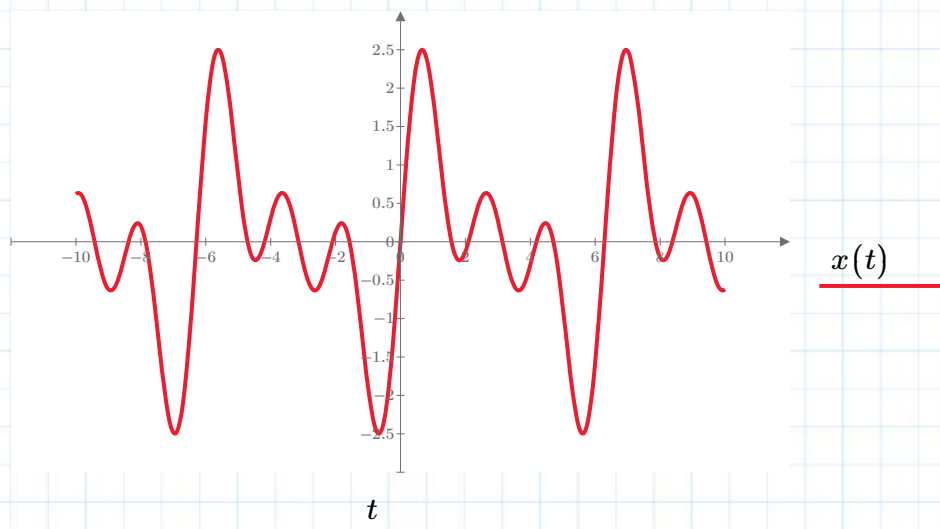


Ex.S2 Response of electric circuit when impulse response and input signal are shown as follows. Sinusoidal waves input.  $R=1\Omega, L=1\text{ H}$  (Series connection)

$$R:=1 \quad L:=1 \quad Z(s):=R+s\cdot L \quad h(t):=e^{-t} \quad \text{impulse response}$$


$$h(t):=e^{-t} \xrightarrow{\text{laplace}} \frac{1}{s+1} \quad H(s):=\frac{1}{s+1} \quad R:=1 \quad \omega:=1 \quad L:=1$$

$$x(t):=\sin(t)+\sin(2\cdot t)+\sin(3\cdot t) \quad \text{input\_signal}$$




$$x_1(t):=\sin(\omega\cdot t) \quad y_1(t):=\frac{1}{\sqrt{R^2+(\omega\cdot L)^2}}\cdot\sin\left(\omega\cdot t-\text{atan}\left(\frac{\omega\cdot L}{R}\right)\right)$$

*output\_signal*

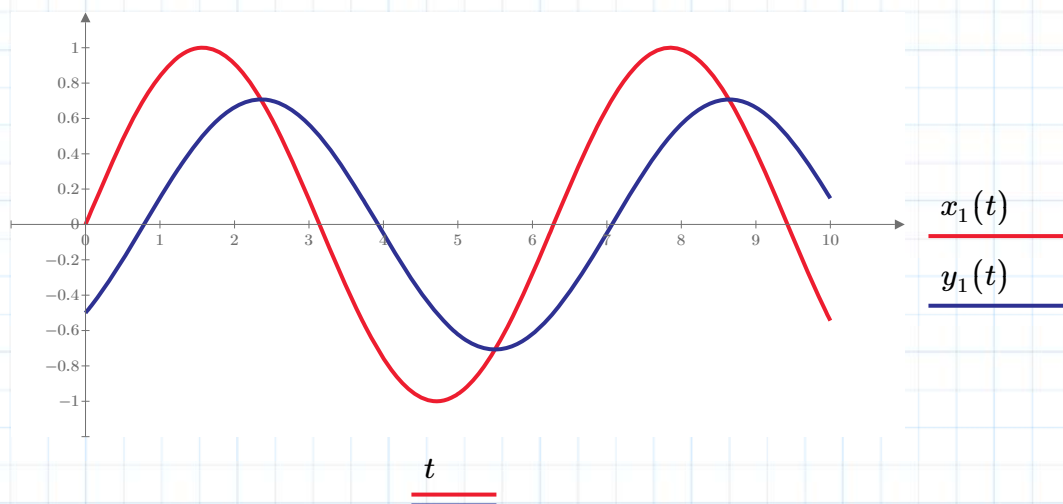

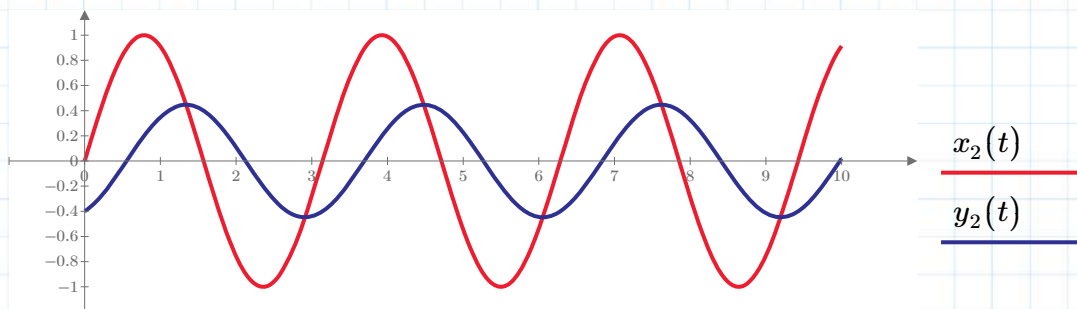
$$x_2(t) := \sin(2 \cdot \omega \cdot t) \quad y_2(t) := \frac{1}{\sqrt{R^2 + (2 \cdot \omega \cdot L)^2}} \cdot \sin\left(2 \cdot \omega \cdot t - \text{atan}\left(\frac{2 \cdot \omega \cdot L}{R}\right)\right)$$




t
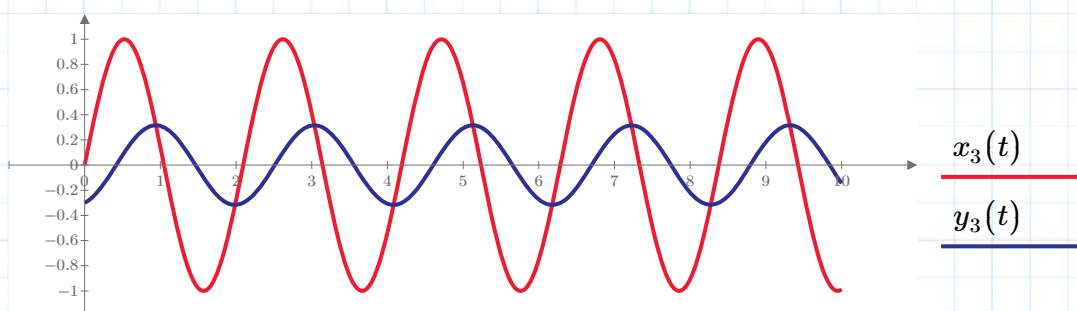
$$x_3(t) := \sin(3 \cdot \omega \cdot t) \quad y_3(t) := \frac{1}{\sqrt{R^2 + (3 \cdot \omega \cdot L)^2}} \cdot \sin\left(3 \cdot \omega \cdot t - \text{atan}\left(\frac{3 \cdot \omega \cdot L}{R}\right)\right)$$



t
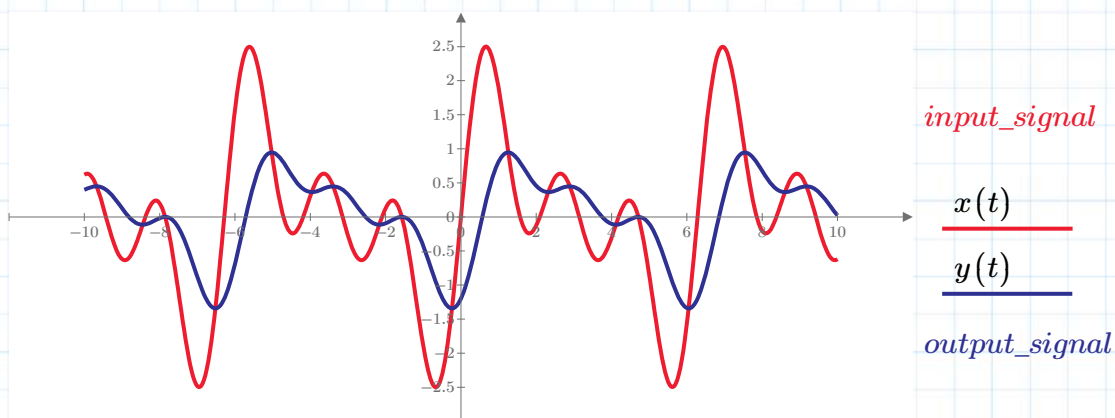
$$x(t) := x_1(t) + x_2(t) + x_3(t) \quad y(t) := y_1(t) + y_2(t) + y_3(t)$$



t

