

Ex.S3 Response of electric circuit when impulse response and input signal are shown as follows. Sinusoidal waves input. $R=1\Omega, L=1\text{ H}$ (Series connection)

$$R:=1 \quad L:=1 \quad Z(s):=R+s\cdot L \quad h(t):=e^{-t} \quad \text{impulse response}$$

$$h(t):=e^{-t} \xrightarrow{\text{laplace}} \frac{1}{s+1} \quad H(s):=\frac{1}{s+1} \quad R:=1 \quad \omega:=1 \quad L:=1$$

$$x(t):=\sin(t)+\sin(2\cdot t)+\sin(3\cdot t) \quad \text{input_signal}$$


$$x_1(t):=\sin(\omega\cdot t) \xrightarrow{\text{laplace}} \frac{1}{s^2+1} \quad X_1(s):=\frac{1}{s^2+1}$$

$$Y_1(s):=X_1(s)\cdot H(s) \rightarrow \frac{1}{(s+1)\cdot(s^2+1)} \xrightarrow{\text{invlaplace}} \frac{e^{-t}}{2} - \frac{\cos(t)}{2} + \frac{\sin(t)}{2}$$

$$x_1(t):=\sin(\omega\cdot t)$$

$$y_1(t):=\frac{e^{-t}}{2} - \frac{\cos(t)}{2} + \frac{\sin(t)}{2}$$

output_signal

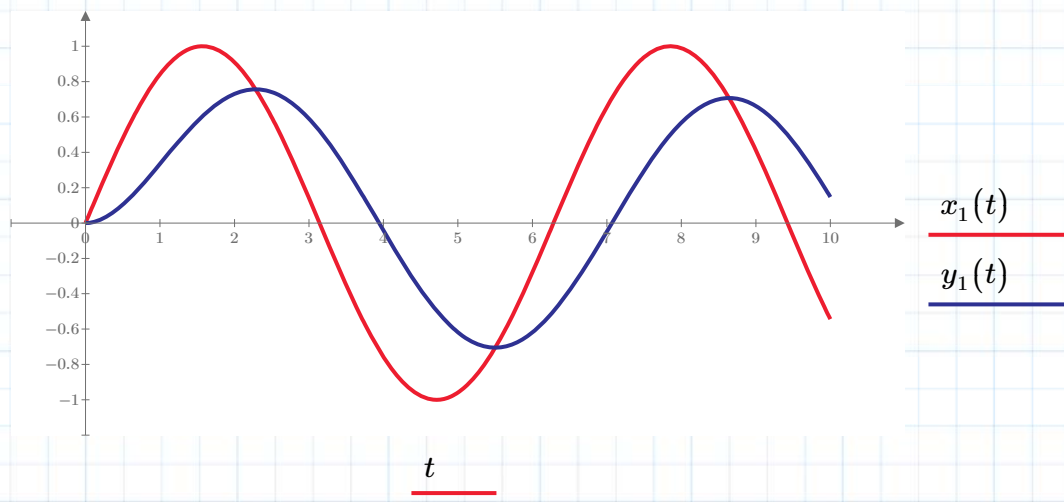


$$x_2(t):=\sin(2\cdot\omega\cdot t) \xrightarrow{\text{laplace}} \frac{2}{s^2+4} \quad X_2(s):=\frac{2}{s^2+4}$$

$$Y_2(s):=X_2(s)\cdot H(s) \rightarrow \frac{2}{(s+1)\cdot(s^2+4)} \xrightarrow{\text{invlaplace}} \frac{2\cdot e^{-t}}{5} - \frac{2\cdot\cos(2\cdot t)}{5} + \frac{\sin(2\cdot t)}{5}$$

$$x_2(t):=\sin(2\cdot\omega\cdot t)$$
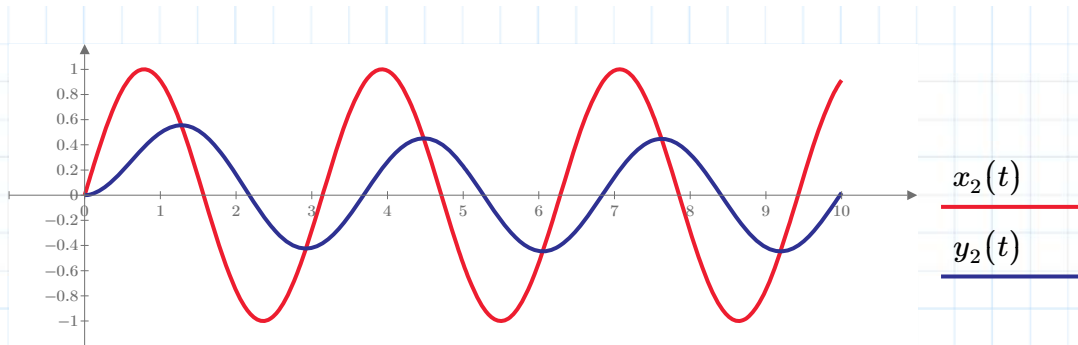
$$y_2(t):=\frac{2\cdot e^{-t}}{5} - \frac{2\cdot\cos(2\cdot t)}{5} + \frac{\sin(2\cdot t)}{5}$$




t

$$x_3(t) := \sin(3 \cdot \omega \cdot t) \xrightarrow{\text{laplace}} \frac{3}{s^2 + 9} \quad X_3(s) := \frac{3}{s^2 + 9}$$

$$Y_3(s) := X_3(s) \cdot H(s) \rightarrow \frac{3}{(s+1) \cdot (s^2 + 9)} \xrightarrow{\text{invlaplace}} \frac{3 \cdot e^{-t}}{10} - \frac{3 \cdot \cos(3 \cdot t)}{10} + \frac{\sin(3 \cdot t)}{10}$$

$$x_3(t) := \sin(3 \cdot \omega \cdot t)$$

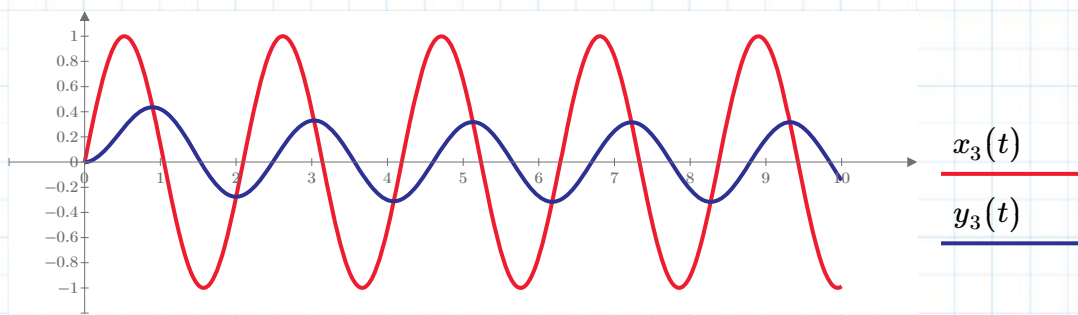
$$y_3(t) := \frac{3 \cdot e^{-t}}{10} - \frac{3 \cdot \cos(3 \cdot t)}{10} + \frac{\sin(3 \cdot t)}{10}$$



t

$$x(t) := x_1(t) + x_2(t) + x_3(t)$$


$$y(t) := y_1(t) + y_2(t) + y_3(t)$$

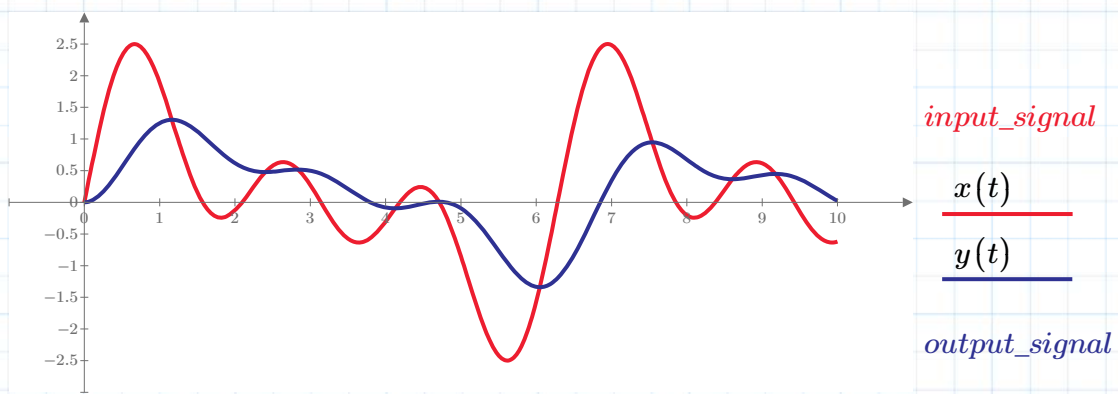

t

input_signal
x(t)
y(t)
output_signal



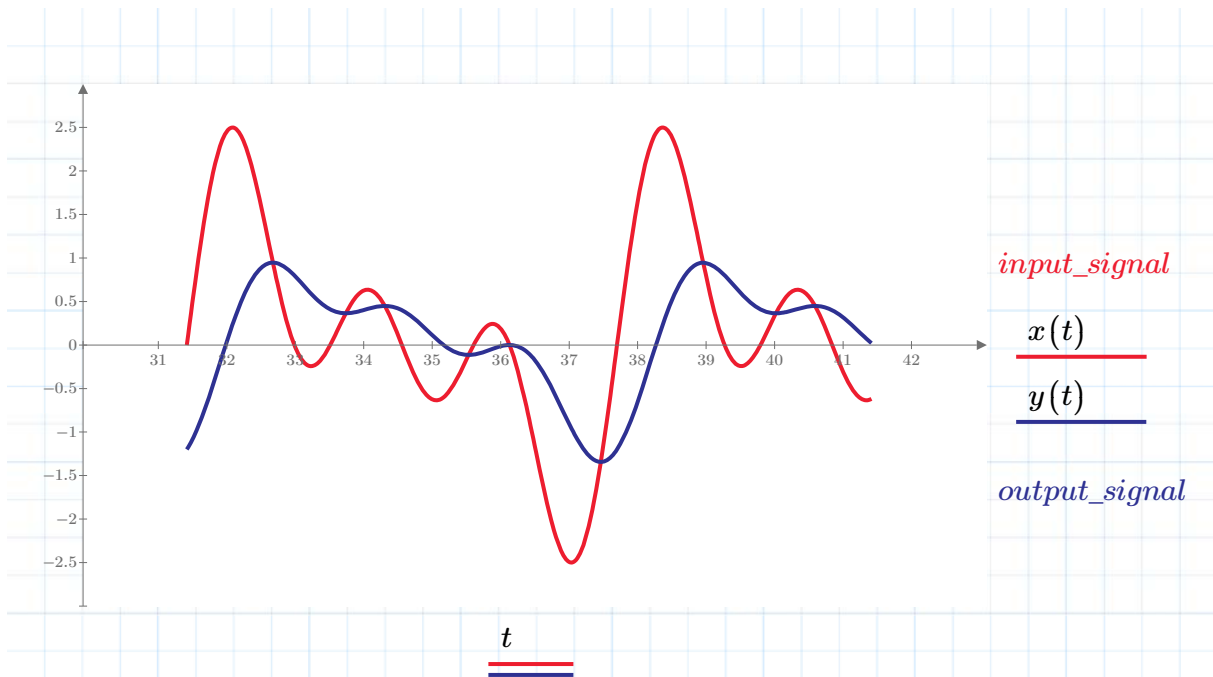

After only 5 cycles, the input and output signals are as same as Ex-s1 or Ex-s2.

$$H(\omega) := \frac{1}{1 + \omega \cdot 1i}$$

$$y_0(t) := |H(1)| \cdot \sin(t + \arg(H(1))) + |H(2)| \cdot \sin(2 \cdot t + \arg(H(2))) + |H(3)| \cdot \sin(3 \cdot t + \arg(H(3)))$$

